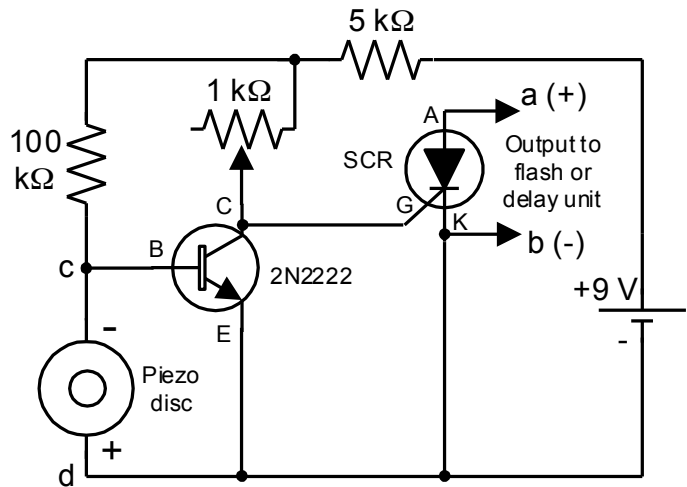


Piezoelectric Sound Trigger Kit

The kit includes parts for a sound trigger that can detect sharp sounds such as handclaps, balloon bursts, and finger snaps. The circuit is sensitive enough to respond to a finger snap from across a room. The trigger can be used to automatically discharge a flash unit.




The circuit diagram is shown to the right. The piezoelectric element responds to sharp sounds. The sensitivity of the trigger is controlled with the 1-k Ω variable resistor. The circuit runs on a 9-V battery, although lower voltages can be used.

A cable must be prepared to connect the output of the trigger to a flash unit. If the flash unit has a PC jack, a PC cord can be spliced to a 2-conductor cable to connect to points *a* and *b* indicated above. If the flash unit doesn't have a PC jack or cord, a hot shoe adapter may be required.



Parts List

- Piezoelectric element (for example, Radio Shack part 273-073)
- 400-V SCR (for example, Digi-Key part EC103D-ND)
- NPN switching transistor (for example, 2N2222)
- 100-k Ω resistor
- 5.1-k Ω resistor
- 1-k Ω potentiometer (A 1-k Ω fixed resistor may be substituted.)
- Battery clip
- 2-conductor cable
- Hook up wire
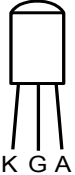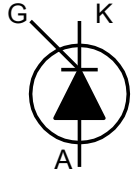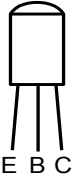
<p style="text-align: center;">SCR pin diagram</p>  <p style="margin-left: 100px;">A = anode (+) K = cathode (-) G = gate</p>	<p style="text-align: center;">SCR circuit symbol</p> 
<p style="text-align: center;">2N2222 transistor</p>  <p style="margin-left: 100px;">E = emitter (-) B = base C = collector (+)</p>	<p style="text-align: center;">Transistor circuit symbol</p> 